

# Simple harmonic oscillation in LC circuits

